

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
DEPARTMENT OF ELECTRICAL ENGINEERING AND COMPUTER SCIENCE

**6.004 Computation Structures**  
Updated Spring 2022

**Quiz #1**


1	/14
2	/13
3	/14
4	/15
5	/14
6	/12

<i>Name</i>	<i>Athena login name</i>	<i>Score</i>
<i>Recitation section</i>		
<input type="checkbox"/> WF 10, 34-302 (Francis)	<input type="checkbox"/> WF 2, 34-302 (Robert)	<input type="checkbox"/> WF 12, 35-310 (Kendall)
<input type="checkbox"/> WF 11, 34-302 (Francis)	<input type="checkbox"/> WF 3, 34-302 (Robert)	<input type="checkbox"/> WF 1, 35-310 (Kendall)
<input type="checkbox"/> WF 12, 34-302 (Grace)	<input type="checkbox"/> WF 10, 35-310 (Sara)	<input type="checkbox"/> opt-out
<input type="checkbox"/> WF 1, 34-302 (Grace)	<input type="checkbox"/> WF 11, 35-310 (Sara)	

**Please enter your name, Athena login name, and recitation section above.** Enter your answers in the spaces provided below. Show your work for potential partial credit. You can use the extra white space and the backs of the pages for scratch work.

 **Problem 1. Static Discipline (14 points)**

The F module below outputs 0.5V when  $0.5 * V_A + V_B > 2V$  for 25ns and outputs 5V when  $0.5 * V_A + V_B < 1.5V$  for 25ns. Furthermore,  $V_A$  and  $V_B$  are both between 0 and 5V. This is summarized in the equation below:



(A) (2 points) If we apply constant  $V_A, V_B$  for 25ns and then measure a  $V_{out} = 5$ , what can we conclude about  $V_B$ ?

- C1:  $V_B < 1.5V$
- C2:  $V_B \leq 2V$
- C3:  $V_B > 2V$
- C4:  $V_B \geq 1.5V$
- C5: None of the above

If  $V_{out} = 5$  then  
 $0.5 * V_A + V_B \leq 2V$   
 $V_B \leq 2V$

Best conclusion about  $V_B$  (Circle one): C1 ... **C2** ... C3 ... C4 ... C5

(B) (2 points) If we apply constant  $V_A, V_B$  for 25ns and then measure a  $V_{out} = 4$ , what can we conclude about  $V_A$ ?

- C1:  $V_A < 3V$
- C2:  $V_A \leq 4V$
- C3:  $V_A > 4V$
- C4:  $V_A \geq 3V$
- C5: None of the above

If  $V_{out} = 4$  then  
 $1.5V \leq 0.5 * V_A + V_B \leq 2V$   
 $V_A \leq 4V$

Best conclusion about  $V_A$  (Circle one): C1 ... **C2** ... C3 ... C4 ... C5

(C) (2 points) What Boolean expression does the F module implement? Specify an equation using A and B.


Boolean Expression: out =      $\overline{A + B}$     

(D) (4 points) What are the parameters that produce a maximum noise immunity for the F module shown above?

$V_{OL} =$    0.5  ,  $V_{IL} =$    1  ,  $V_{IH} =$    4  ,  $V_{OH} =$    5  

Noise Immunity =   0.5

 (E) (4 points) Now suppose we have a new device G, whose voltage transfer characteristic (VTC) is depicted below. We want to use both F and G in the same circuit, but we want to use the same signaling specification for both devices. What are the parameters that will produce a maximum noise immunity while satisfying both devices?




$$V_{OL} = \underline{0.5}, V_{IL} = \underline{0.75}, V_{IH} = \underline{4.25}, V_{OH} = \underline{5}$$

$$\text{Noise Immunity} = \underline{0.25}$$

**Problem 2. Boolean Algebra and Combinational Logic (13 points)**

 (A) (2 points) Consider the schematic of the circuit  $F(A, B, C)$  below. Derive its truth table.



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

(B) (3 points) Find the normal form and a minimal sum-of-products expression for  $G(A, B, C)$ .

A	B	C	G
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

1. Normal form for  $G = \underline{\hspace{2cm}} \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}bc + a\bar{b}c + abc \underline{\hspace{2cm}}$

2. Minimal sum of products for  $G = \underline{\hspace{2cm}} c + \bar{a}\bar{b} \underline{\hspace{2cm}}$

$$\bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}bc + a\bar{b}c + abc = \bar{a}\bar{b}\bar{c} + \bar{a}c + ac = \bar{a}\bar{b}\bar{c} + c = c + \bar{a}\bar{b}$$

(C) (2 points) Is the circuit  $G(A, B, C)$  functionally complete? Explain.

$F$  is functionally complete as we can construct a NOR gate.  $F(A, B, 0) = \text{NOR}(A, B)$ .

(D) (4 points) Simplify the following Boolean expressions by finding a minimal sum-of-products expression for each one. (Note: These expressions can be reduced into a minimal SOP by repeatedly applying the Boolean algebra properties we saw in lecture.)

$$1. (x + y)(x + \bar{y})(\bar{x} + z)(\bar{x} + \bar{z}) = (x + xy + x\bar{y} + y\bar{y})(\bar{x} + \bar{x}z + \bar{x}\bar{z} + z\bar{z}) \\ = x\bar{x} = 0$$

$$2. (x + y + z)(x + \bar{y} + \bar{z}) = x + x\bar{y} + x\bar{z} + xy + y\bar{y} + y\bar{z} + xz + \bar{y}z + z\bar{z} \\ = x + y\bar{z} + \bar{y}z$$

(E) (2 points) For each of the expressions in part D, find a set of variable assignments that makes the expression true or explain why the expression cannot be satisfied with any variable assignment.


1.  $x = \underline{\quad}, y = \underline{\quad}, z = \underline{\quad}$  or UNSATISFIABLE.

2.  $x = \underline{1}, y = \underline{0}, z = \underline{0}$  or UNSATISFIABLE.

1xx, x10, and x01 are all valid solutions.

**Problem 3: CMOS (14 points)**

 
(A) (3 points) The following 5-input circuit consists of two 2-input NAND gates, an inverter, and a 3-input AND gate. Write a Boolean expression for the function Z. If the function Z can be implemented using a **single CMOS gate**, please draw the corresponding single CMOS gate. **For full credit, use a minimum number of FETs.** If it cannot be implemented using a single CMOS gate, **explain why not.**



$$Z(A, B, C, D, E) = (\overline{AB})(\overline{C})(\overline{DE}) = (\overline{A} + \overline{B})(\overline{C})(\overline{D} + \overline{E})$$

The function Z is inverting (note we can express Z as a function of only the negations of the inputs) so we can implement Z using a single CMOS gate.

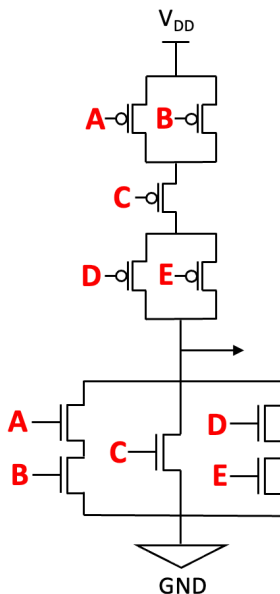Pullup (pFETs): (A in parallel with B) in series with C in series with (D in parallel with E)  
 Pulldown (nFETs): (A in series with B) in parallel with C in parallel with (D in series with E).



(B) (3 Points) A single CMOS gate, consisting of an output node connected to a single pFET-based pullup circuit and a single nFET-based pulldown circuit (as described in lecture), computes  $F(A, B, C, D)$ . It is observed that  $F(0, 1, 1, 1) = 1$ . What can you say about the following values? **Circle one of the options (0, 1, can't tell).**

a.  $F(1, 1, 0, 1) = 0 \dots 1 \dots$  **can't tell**

This has both rising and falling inputs compared to the reference we are given, so we can't predict what will happen to the output.

b.  $F(0, 1, 0, 0) = 0 \dots$  **1**  $\dots$  can't tell

This has falling inputs compared to the reference, so the output must either stay the same or rise. Since the reference output is 1 the output cannot rise, so it must stay the same.


c.  $F(1, 1, 1, 1) =$  **0**  $\dots 1 \dots$  can't tell

An inverting function (a single CMOS gate can only implement inverting functions) must output 0 when the input is all 1s.

(C) (8 Points) For each of the following Boolean functions, choose the appropriate pullup design, i.e., the one which, properly connected, implements that gate's pullup using the **minimum number of active transistors** (a FET that is never on is not active). You can connect one of the inputs (A, B, C, or D) or a constant (GND, or VDD) to each pFET.

For each expression, circle the name of your chosen pullup design (e.g. PU1) and label each pFET in your chosen design with the appropriate input or constant. You can use a design more than once. If none of the above pullups implements the function's pullup, circle "NONE".

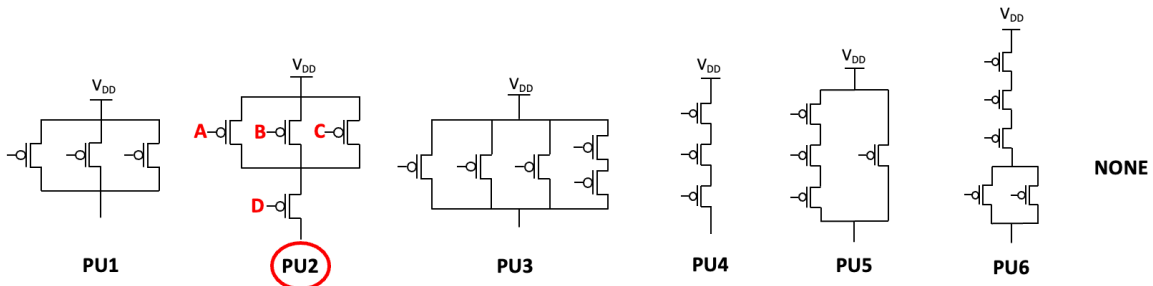a.  $F(A, B, C, D) = (\overline{ABC})\overline{D}$




$$F(A, B, C, D) = (\overline{ABC})\overline{D} = (\overline{A} + \overline{B} + \overline{C})\overline{D}$$

The pullup circuit has (A in parallel with B in parallel with C) in series with D.



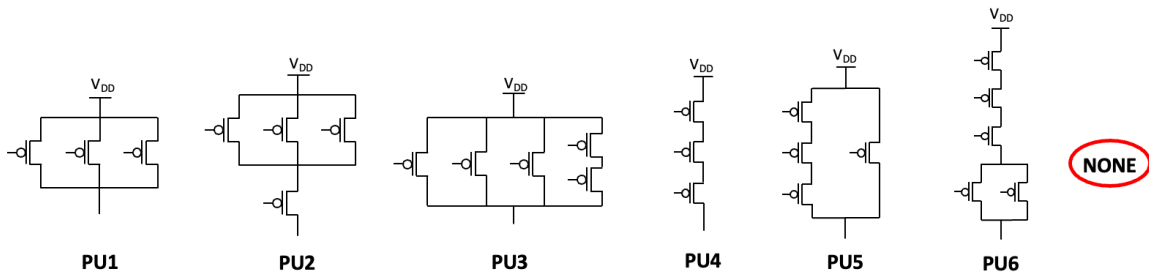
b.  $F(A, B, C, D) = \overline{(A + B)(\bar{C} + \bar{D})}$



$F(A, B, C, D) = \overline{(A + B)(\bar{C} + \bar{D})} = \overline{A + B + \bar{C} + \bar{D}} = \bar{A}\bar{B} + CD$

This function is non-inverting (note the presence of C and D in the expression for F) so the answer is NONE.

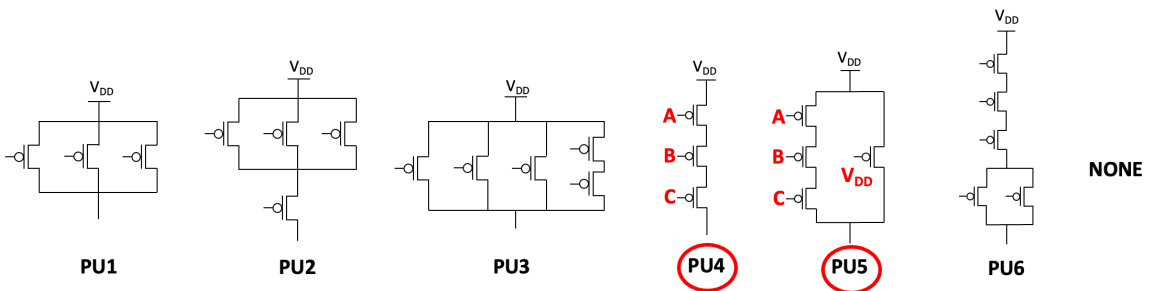
c.  $F(A, B, C, D) = \overline{(B + C)(\bar{A})(\bar{B}\bar{D})}$



$F(A, B, C, D) = \overline{(B + C)(\bar{A})(\bar{B}\bar{D})} = \overline{\bar{B}\bar{C}\bar{A}(\bar{B} + \bar{D})} = \overline{\bar{B}\bar{C}\bar{A}\bar{B} + \bar{B}\bar{C}\bar{A}\bar{D}} = \overline{\bar{B}\bar{C}\bar{A} + \bar{B}\bar{C}\bar{A}\bar{D}} = \overline{\bar{B}\bar{C}\bar{A}(1 + \bar{D})} = \overline{\bar{B}\bar{C}\bar{A}}$

The pullup circuit has A, B, and C all in series. This can be implemented using PU4, or using PU5 with the additional parallel pFET connected to  $V_{DD}$  (both solutions have the same number of active transistors since the pFET connected to  $V_{DD}$  is never on).

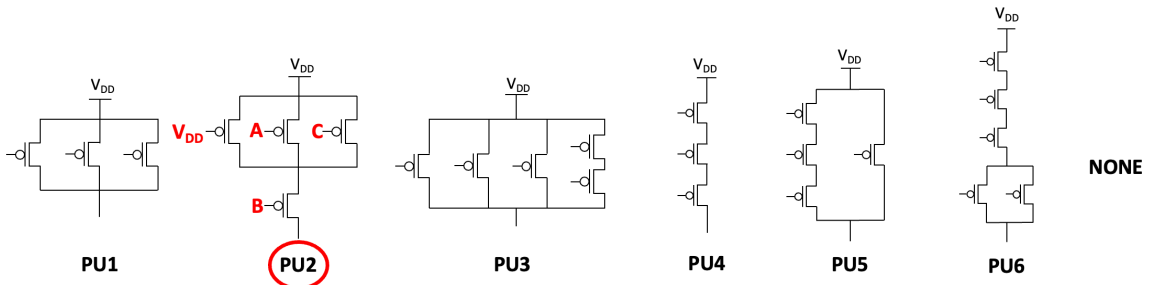d.  $F(A, B, C, D) = \overline{(\bar{A} + \bar{C})(\bar{B})(D + \bar{D})}$



$F(A, B, C, D) = \overline{(\bar{A} + \bar{C})(\bar{B})(D + \bar{D})} = \overline{(\bar{A} + \bar{C})(\bar{B})}$

The pullup circuit has (A in parallel with C) in series with B. This can be implemented using PU2 by connecting the extra parallel pFET to  $V_{DD}$ .

**Problem 4. Combinational Circuits (15 points)**


(A) (2 points) Fill out the truth table for the 3-input parity function parity that returns true if an odd number of bits are true.

x[0]	x[1]	x[2]	out
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(B) (2 points) Implement the function above in Minispec.

```
function Bit#(1) parity3(Bit#(3) x);  
    return x[0] ^ x[1] ^ x[2];  
endfunction
```

 
(C) (6 points) Determine whether each of the following circuits implements the parity3 function. **If it does not, change one gate in the circuit to have it implement parity3.**



Implements the function parity:

**YES**

NO

 

Implements the function parity:

YES

**NO**


XOR should be replaced with XNOR, or OR should be replaced with NOR.

(D) (5 points) Implement the parametric function parity#(n) in Minispec, which computes the parity of an n-bit input, returning 1 if and only if an odd number of bits are 1. **For full credit, parity#(n) must have logarithmic delay with respect to n. n is greater than or equal to 1, and not necessarily a power of two.**

```
function Bit#(1) parity#(Integer n) (Bit#(n) x);
    if (n == 1) begin
        return x
    end else begin
        return parity#(n/2)(x[n/2-1:0]) ^ parity#(n-n/2)(x[n-
1:n/2]);
    end
endfunction
```

**Problem 5. Combinational and Sequential Logic Timing (14 points)**

 (A) (3 points) Given the timing parameters in the table below, what is the propagation delay of this circuit?




Gate	$t_{pd}$ (ns)	$t_{cd}$ (ns)
OR2	4	1.5
INV	2	1
AND2	3	2

Propagation delay (ns):   9  

**Longest Path goes through INV + AND2 + OR2 = 2 + 3 + 4 = 9**

 (B) (6 points) Given the timing parameters in the table below, please indicate whether or not each constraint is satisfied by the circuit below, and explain your answer. All registers are driven by a common clock with period  $t_{clk} = 10\text{ns}$ .



Component	$t_{pd}$ (ns)	$t_{cd}$ (ns)	$t_{SETUP}$ (ns)	$t_{HOLD}$ (ns)
Register (R1, R2, R3, R4)	5.5	1	2	1.5
Combinational Logic (CL1, CL2)	2.5	1	N/A	N/A

Setup time constraint (select one):

SATISFIED

NOT SATISFIED

Explanation:

**R2 -> R2:  $t_{PD,R2} + t_{PD,CL1} + t_{PD,CL2} + t_{Setup,R2} = 5.5 + 2.5 + 2.5 + 2 = 12.5 > t_{CLK} = 10\text{ns}$  so setup constraint is not satisfied.**

Hold time constraint (circle one):

SATISFIED

NOT SATISFIED

Explanation:

**R3 -> R4:  $t_{CD,R3} = 1 > t_{Hold,R4} = 1.5$  so hold time not satisfied.**

(C) (5 points) We would like for the circuit from (B) to be able to function with a clock period of 9ns. Using the replacement parts below, modify the circuit so that it can operate using a clock period of 9ns *while satisfying the setup and hold time constraints*. For full credit, minimize the number of replacements made.

Component	$t_{pd}$ (ns)	$t_{cd}$ (ns)	$t_{SETUP}$ (ns)	$t_{HOLD}$ (ns)
Register-New	3	2	2	0.5
CombinationalLogic-New	2	0.5	N/A	N/A

CL1: **REPLACED (with CombinationalLogic-New)** NOT REPLACED

CL2: **REPLACED (with CombinationalLogic-New)** NOT REPLACED

R1: **REPLACED (with Register-New)** NOT REPLACED

R2: **REPLACED (with Register-New)** NOT REPLACED

R3: REPLACED (with Register-New) **NOT REPLACED**

R4: **REPLACED (with Register-New)** NOT REPLACED

**Replace R3 instead of R4 is also valid.**

**To satisfy the setup time on the R2 -> R2 path, we need  $t_{PD,R2} + t_{PD,CL1} + t_{PD,CL2} + t_{Setup,R2} \leq 9ns$ .**

**Since  $t_{Setup,R2}$  is not changing this means that the first 3 terms must sum to less than or equal to 7. The only way to achieve this is to replace R2, CL1, and CL2.**

**Next, we check the R1 -> R2 path which is  $t_{PD,R1} + t_{PD,CL2} + t_{Setup,R2} \leq 9ns$ . So  $t_{PD,R1} + t_{PD,CL2}$  must be less than or equal to 7. If we keep the old R1, then this adds up to 9.5 which does not satisfy the necessary constraints, so we also need to replace R1.**

**With these changes in place the R2 -> R3 and the R3 -> R4 setup time constraints are also satisfied.**

**Finally, looking at the R3 -> R4 path, we see that without any changes the hold time constraint is not satisfied because  $t_{CD,R3} = 1 < t_{Hold,R4} = 1.5ns$ . So, we either need to**


**replace R3 or R4. Either one will result in satisfying the hold time constraint as well as the setup time constraint.**

**If we replace R3:  $t_{CD,R3} = 2 > t_{Hold,R4} = 1.5ns$ .**

**If we replace R4:  $t_{CD,R3} = 1 > t_{Hold,R4} = 0.5ns$ .**

 **Problem 6. Finite State Machines (12 points)**

Consider the following finite state machine. The initial state is A. The output of B is 1 and the output of all other states is 0.



(A) (3 points) Given the following inputs, determine what the next state will be after the last input is processed. Assume the FSM starts at initial State A for each series of inputs.

(i) 00010

Final state:     **B**    

(ii) 010000001

Final state:     **C**    

(iii) 010101010011111011101110101

Final state:     **C**    

(B) (3 points) For the second sequence of inputs in the question above (copied below), determine what the outputs are for each cycle. Note that the FSM starts in State A in Cycle 1.

Cycle	1	2	3	4	5	6	7	8	9
Input	0	1	0	0	0	0	0	0	1
Output	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>
Current State	<b>A</b>	<b>A</b>	<b>B</b>	<b>B</b>	<b>B</b>	<b>B</b>	<b>B</b>	<b>B</b>	<b>B</b>

(C) (4 points) To encode the states, two bits  $S_1$  and  $S_0$  are used. States A, B, and C are encoded with bits 00, 01, and 10, respectively. Determine truth table for the FSM.

$S_1^t$	$S_0^t$	input	$S_1^{t+1}$	$S_0^{t+1}$	output
0	0	0	<b>0</b>	<b>0</b>	<b>0</b>
0	0	1	<b>0</b>	<b>1</b>	<b>0</b>
0	1	0	<b>0</b>	<b>1</b>	<b>1</b>
0	1	1	<b>1</b>	<b>0</b>	<b>1</b>
1	0	0	<b>1</b>	<b>0</b>	<b>0</b>
1	0	1	<b>1</b>	<b>0</b>	<b>0</b>



(D) (2 points) Find the minimal sum-of-products expression for the output.

output =  $\overline{S_1}S_0$  or  $S_0$

**END OF QUIZ 1!**